



Computer Architecture I - WS 02/03
 (due: 11.11.2002)

Excercise 1: (Compound Adder) (5+3+2 points)

In figure 1 you see the recursive Definition of a compound adder with inputs $a[n - 1 : 0]$ and $b[n - 1 : 0]$ ¹. This circuit computes simultaneously $s^0 = \langle a \rangle + \langle b \rangle$ and $s^1 = \langle a \rangle + \langle b \rangle + 1$.

1. Compute cost and delay of a n bit compound adder in a closed formula². Cost and delay of the basic gates (AND, OR, XOR, XNOR) are 1. Cost of a n bit multiplexer is $3n$. Its delay is 2.
2. Proof the correctness of your formulas by induction.
3. Compound adders can be used to construct conditional sum adders. Give a recursion construction (draw a figure) of a n bit conditional sum adder which uses compound adders.

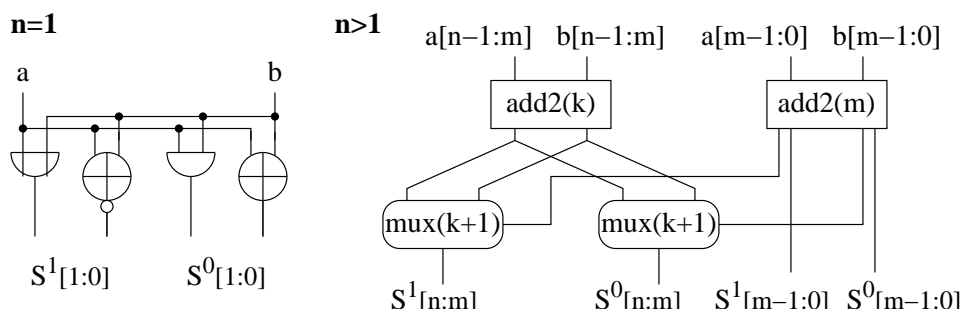


Figure 1: Compound Adder

Exercise 2: (Cyclic Left Shifter) (3 + 3 points)

For string $a[n - 1 : 0]$ and natural numbers $i \in \{0, \dots, n - 1\}$ we consider the functions

$$\begin{aligned}
 cls(a, i) &= (a[n - i - 1] \dots a[0]a[n - 1] \dots a[n - i]) \\
 crs(a, i) &= (a[i - 1] \dots a[0]a[n - 1] \dots a[i])
 \end{aligned}$$

The function $cls(a, i)$ is called a *cyclic left shift*, the function $crs(a, i)$ is called a *cyclic right shift*. For a constant i we can construct a cyclic left shifter by the construction show in figure 2. The input i is called the shift distance of the shifter.

1. Give a construction of a n bit cyclic left shifter for arbitrary i with $0 \leq i < n$. This shifter should use $\log(n)$ cyclic left shifters with fixed shift distance.

¹Gates with a point at their lower end are negated. e.g. For $n = 1$ S^1 is computed by an OR and a XNOR gate.

²You can assume that n is a power of two.

 


Figure 2: Cyclic Left Shifter for a constant i

2. How can you build a cyclic right shifter using a cyclic left shifter? Why is your solution correct?

Exercise 3: (Binary Representation)

(3 + 3 points)

1. Show that there is only one binary representation for a given number a (if one cuts away leading zeros).
2. Let a and b be n bit binary numbers: $a, b \in \{0, 1\}^n$.

Let $<_{lex}$ be defined by:

- $n = 1$: $a <_{lex} b \iff a[0] = 0 \wedge b[0] = 1$
- $n > 1$: $a <_{lex} b \iff a[n-1] <_{lex} b[n-1] \vee (a[n-1] = b[n-1] \wedge a[n-2:0] <_{lex} b[n-2:0])$

Proof the following claim:

$$\langle a \rangle < \langle b \rangle \iff a <_{lex} b.$$

Exercise 4: (realistic cost model)

(8 points)

For this exercise we will use the following cost and delay model:

- Components are placed on a regular grid (see figure 3).

 


Figure 3: Grid Cost Model

- A simple gate has size 1x1: it uses one cell of the grid.
- Connections between gates also use cells. Connections can leave cells at the upper, lower, right or left side, but not at the corners.

- The cost of a circuit is the number of cells which are used by gates and connections of the circuit.
- The delay of a simple gate is one. The delay of a connection cell is also one. The delay of a circuit is the maximum delay between some input and some output of the circuit.

For the example in figure 3 (a one bit multiplexer) we have cost 9 and a delay of 7.

Find a circuit for an n bit OR tree³. Give a recursive definition of your circuit. Design your circuit for speed (small delay). The faster your circuit is the more points you will get.

³An OR tree with input $a[n - 1 : 0]$ outputs a 1 if any of the input bits is 1: $o = a[n - 1] \vee \dots \vee a[0]$.