## Saarland University Department 6.2 - Computer Science Prof. Dr. W. J. Paul M. Sc. Christian Müller

## Computer Architecture I - WS 07/08 Exercise Sheet 2

### **Organizational stuff**

**Important!** To receive credit points for this course, students of CS and CuK must register for it in the  $HISPOS^1$  system of the examination office by December 1, 2007.

### Excercise 1: (circuit definition, graph theory)

- 1. Get familiar with the formal definition of a  $graph.^2$
- 2. Consider the following circuit S consisting of an inverter, of an AND, NAND and of a NOR gate.



Let a, b, c be inputs and d, e outputs of S. Describe S formally as a graph, i.e. show the set of its edges, nodes, etc.

3. Give the in/out-degree numbers of each node.

### Excercise 2: (circuit definition)

The depth de(g) of a gate g in a circuit S is defined as follows:

$$de(g) = \begin{cases} 0 & : g \text{ is an input of } S \\ max\{l(p) \mid p \text{ is a path into } g \text{ in } S\} & : \text{ otherwise} \end{cases}$$

Where l(p) is the length of a path p defined over the number of gates in p. Prove that into a gate of depth u there are at most  $3^u$  paths.

### Excercise 3: (decomposition lemma)

Let  $a \in \mathbb{B}^n$  and  $\langle a \rangle$  its binary representation. For  $k \in \{0, \ldots, n-1\}$  prove:

$$\langle a[n-1:0] \rangle = \langle a[n-1:k] \rangle \cdot 2^k + \langle a[k-1:0] \rangle$$

<sup>&</sup>lt;sup>1</sup>https://www.lsf.uni-saarland.de

<sup>&</sup>lt;sup>2</sup>You can use, e.g., Wikipedia or a lot of computer science books.

Saarland University Department 6.2 - Computer Science Prof. Dr. W. J. Paul M. Sc. Christian Müller

# Computer Architecture I - WS 07/08

Exercise Sheet 2

### Excercise 4: (sign extension)

Let  $a \in \mathbb{B}^n$  and  $\langle a \rangle$  its binary representation. Prove that  $\langle a \rangle = \langle 0^n a \rangle$  for  $n \in \mathbb{N}$ .

### Excercise 5: (full adder)

Full adder is a circuit computing the sum of three input bits:

$$fa: \mathbb{B}^3 \to \mathbb{B}^2, fa(a, b, c) = (s_1, s_0)$$

with  $\langle a \rangle + \langle b \rangle + \langle c \rangle = \langle s_1 s_0 \rangle$ . E.g., f(0, 0, 0) = (0, 0), f(0, 1, 0) = f(1, 0, 0) = (0, 1), f(1, 0, 1) = (1, 0), etc. Implement this circuit using logical gates.

#### Excercise 6: (carry chain adder)

Consider the implementation of a *carry chain adder*.<sup>3</sup> Prove that the carry chain adder computes the following function cca:

$$cca: \mathbb{B}^n \times \mathbb{B}^n \times \mathbb{B} \to \mathbb{B}^{n+1}$$
$$cca(a[n-1:0], b[n-1:0], c_{in}) = c_{out}s[n-1:0]$$

with  $\langle a[n-1:0] \rangle + \langle b[n-1:0] \rangle + \langle c_{in} \rangle = \langle c_{out}s[n-1:0] \rangle$  where  $c_{out}s[n-1:0]$  is just a concatenation of bit  $c_{out}$  and bitvector s[n-1:0].

### Excercise 7: (carry save (or 3/2) adder)

Carry Save Adder<sup>4</sup> (or also called "3/2 adder") is a circuit computing the following function:

$$\begin{aligned} csa: \mathbb{B}^n \times \mathbb{B}^n \times \mathbb{B}^n \to \mathbb{B}^{n+1} \times \mathbb{B}^{n+1} \\ csa(a[n-1:0], b[n-1:0], c[n-1:0]) &= (s[n:0], t[n:0]) \end{aligned}$$

with  $\langle a[n-1:0] \rangle + \langle b[n-1:0] \rangle + \langle c[n-1:0] \rangle = \langle s[n:0] \rangle + \langle t[n:0] \rangle$ . Prove this.

**Hint**: use the decomposition lemma (exercise 3) in order to transform the sum of three bitvectors into a sum of two bitvectors. Argue that the carry save adder realizes the same transformation.

### Excercise 8: (O-notation)

- 1. Get familiar with the O-notation.
- 2. Give the definitions of sets  $\mathcal{O}(f), o(f), \Omega(f), \omega(f), \Theta(f)$  for some function f.
- 3. Which of the following statements are true and which are not. Explain!

(a) 
$$n^2 \cdot log(n) \in o(n \cdot log(n)^3)$$

(b) 
$$\frac{n^2-n}{4} \in \mathcal{O}(n^2)$$

(c) 
$$n^{10!} \in \omega(2^n)$$

(d)  $\forall f : \mathcal{O}(f) \cap \Omega(f) = \Theta(f)$ 

<sup>&</sup>lt;sup>3</sup>Take a look into your lecture notes or into [MP00] (Figure 2.11).

<sup>&</sup>lt;sup>4</sup>Figure 2.26 in [MP00] or your lecture notes.