

Computer Architecture – WS14/15
Exercise Sheet 2 (due: 11.11.14, 26 points)

Exercise 1: (computational limits) (4 points)

Estimate the physical limit for the computational frequency of a processor made out of one spoon of water. Hint: use the uncertainty principle and the mass-energy equivalence.

Exercise 2: (smart decoder) (6 points)

Give a construction of a “smart” decoder, i.e. a circuit which fulfills the following specification:

- input $x \in \mathbb{B}^n$
- output $y \in \mathbb{B}^{2^n}$, s.t.

$$y[i] \leftrightarrow \langle x \rangle = i$$

Prove that your construction

- (a) mets the specification.
- (b) has a delay logarithmic in n .

Exercise 3: (fast OR-trees) (4 points)

Let $n = 2^k$ for $k > 0$. Construct a circuit which implements the following function:

$$\begin{aligned} or & : \mathbb{B}^n \rightarrow \mathbb{B} \\ or(a_{n-1}, \dots, a_0) & = \bigvee_{i=0}^{n-1} a_i \end{aligned}$$

Optimize the delay of your construction using gates from

- (a) the upper half of table 1.
- (b) the entire table 1.

gate	symbol	cost	delay
INV	\neg	1	1
AND	\wedge	2	2
OR	\vee	2	2
NAND	$\overline{\wedge}$	2	1
NOR	$\overline{\vee}$	2	1
XOR	\oplus	4	2

Table 1: Cost and delay of gates

Exercise 4: (circuit definition) (4 points)

Consider the circuit in figure 1, consisting of an inverter, of an AND, NAND and of a NOR gate. Let a, b, c be inputs and d, e outputs of S .

- (a) Describe S formally as a graph, i.e. show the set of its edges, nodes, etc.
- (b) Give the in/out-degree numbers of each node.

 


Figure 1: Circuit S

Exercise 5: (SRAM construction) (8 points)

Recall the principles of static RAM construction from the lecture.

- Specify and construct an (n, a) -RAM with two ports A and B which can both be used to read and write. In case of simultaneous writes to the same address the write specified by port A should win.
- Provide an extra control input inv . Activation of inv sets all register contents to 0^n and overrides possible concurrent ordinary writes¹.

¹Such RAMs are used for instance to store the status of cache lines. Invalid data is signaled by value 0^n . After power up caches contain no meaningful data, and this is signaled in their status if one activates inv together with *reset*.